

Ultra-low Impedance (20 micro ohm) Measurement using 2-Port Shunt-Through

Measuring ultra-low impedance is a challenge for any power distribution network (PDN) design engineer. The 2-port shunt-through measurement is the standard method for measuring milliohm impedances up to very high frequencies (GHz). Unfortunately, this measurement includes an undesirable ground loop related to the instrument grounds and test setup cabling. The ground loop introduces significant errors if proper care is not taken. This application note shows how to measure as low as 20 $\mu\Omega$ using the Picotest [J2102A](#) as a ground loop breaker.

[Figure 1](#) shows the measurement set up to measure impedance in 2-port shunt-through configuration using the Keysight [E5061B](#) vector network analyzer (VNA) and Picotest ground isolators - either [J2102A](#) or [J2113A](#). Picotest solutions work with any commercial VNA, oscilloscope, or spectrum analyzer. The [J2102A](#) (common mode transformer) is used to measure impedances at and above 20 $\mu\Omega$. [J2113A](#) (semi-floating differential amplifier) can be used to measure impedances at or above 1 m Ω . The [J2113A](#) is effective down to DC, while the [J2102A](#) is effective at, or even below, 100 Hz. This application note describes the measurement at or above 20 $\mu\Omega$, and the measurements use [J2102A](#) which are effective at or above 100 Hz.

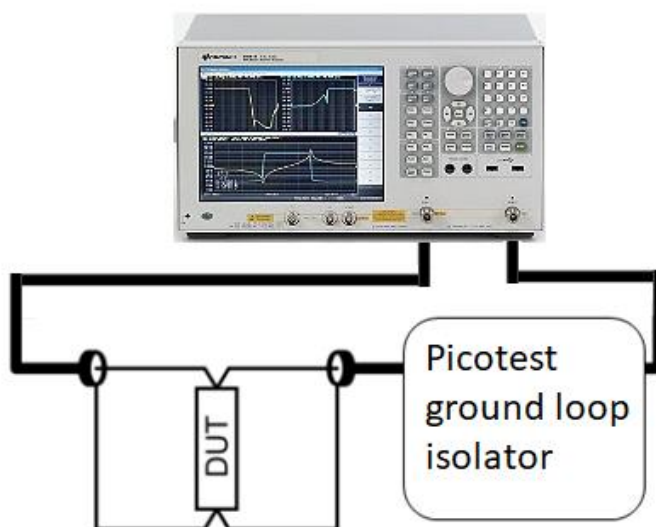


Figure 1: 2-port shunt-through impedance measurement setup using the Keysight [E5061B](#) VNA and the Picotest ground isolators [J2102A/J2113A](#).

Basic theory of the 2-port shunt-through measurement

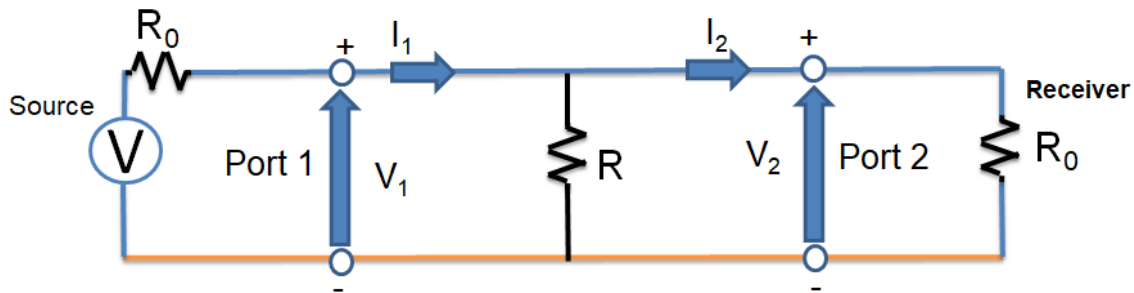


Figure 2: Circuit diagram of 2-port shunt-through measurement to measure R.

[Figure 2](#) shows the circuit configuration to measure a small valued resistor in 2-port shunt-through measurement. From the definition of S_{21} [[1](#), pp. 2-3],

$$S_{21} = \frac{V_2 + I_2 R_0}{V_1 + I_1 R_0} = \frac{2R}{2R + R_0} \quad (1)$$

Solving for R we get,

$$R = \frac{25 \cdot S_{21}}{1 - S_{21}} \simeq 25 \cdot S_{21} \quad (2)$$

where it is assumed that $R_0 = 50 \Omega$ and $S_{21} \ll 1$ (True for very small impedance magnitudes/resistances - $R \ll R_0$). [Equation 1](#) is less intuitive in 2-port shunt-through measurements. Another representation of the definition of S_{21} is shown in [[1](#), pp. 2],

$$S_{21} = \sqrt{\frac{\text{Power absorbed by Receiver when R is present}}{\text{Power absorbed by Receiver when R is absent}}} = \frac{2R}{2R + R_0} \quad (3)$$

After simplification, [Equation 3](#) results in the same value for S_{21} . The difference here is that [Equation 3](#) gives an intuitive feeling for what is happening with S_{21} compared to [Equation 1](#). The denominator (= Power absorbed by Receiver when R is absent) is constant for a VNA, if the source and receiver impedances are fixed. One exception to this is proposed by Steve Sandler in his paper “Extending the usable range of the 2-port shunt-through impedance measurement” [[2](#)]. Here the source R_0 is increased to shift the measurement window. The source and receiver R_0 are increased to a higher value by adding an external resistor say, 450 Ω . The R_s now becomes 500 Ω for a 50 Ω VNA assuming that the frequency range we are interested in is such that the external resistor is electrically very small and is a lumped element at that frequency. This method effectively reduced the maximum power that can be sourced from a VNA, which increases the range of impedances that can be measured. It should be noted that the sensitivity is an inherent property of a VNA, and is not changed here.

This means that the minimum measurable value and maximum measurable value are both increased.

In [Equation 3](#), S_{21}^2 is the received power in Rx scaled by the power that could have been received if the DUT was not present. Let us look at the effect of this in 2-port impedance measurements. $R = 25 \cdot S_{21}$, and S_{21} increases when the received power increases.

Any increase in the received power will be reflected or sensed by the VNA measurement system as an increase in the DUT resistance, R. This is important in understanding the ground loop problem.

Non-idealities and the Inherent Ground Loop

Like all other measurements, the 2-port shunt-through measurements also suffer from non-idealities. [Figure 3](#) shows two non-idealities,

1. Cable losses
2. Ground loop

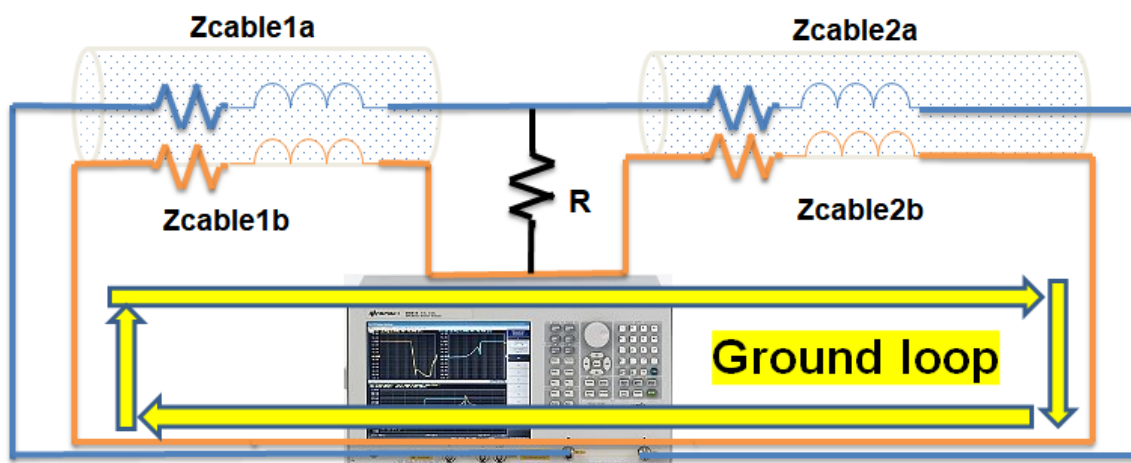


Figure 3: Non-idealities added in the 2-port shunt-through measurements.

Every cable will have cable losses which are marked as cable resistances in [Figure 3](#). Due to National Electrical Code (NEC) requirements for public safety, all grounds in a VNA have to be connected together. This forms a ground loop in the 2-port shunt-through measurements as shown in [Figure 3](#).

[Figure 4](#) shows an alternate path for signal current return, referred to as common mode current. The addition of ground connections created this path. If this path never existed, all the current would have returned through the cable. The new path created an additional path for current which depends upon the value of Z_g . In almost all VNAs, $Z_g \ll Z_{cable1b}$ and $Z_{cable2b}$. So the additional current is much larger compared to the case of not having this additional path. This additional current adds more power in the Receiver which causes to increase S_{21} and in turn the estimated R which $25 \cdot S_{21}$. This is an error in measurements, and does not relate to the actual value of R.

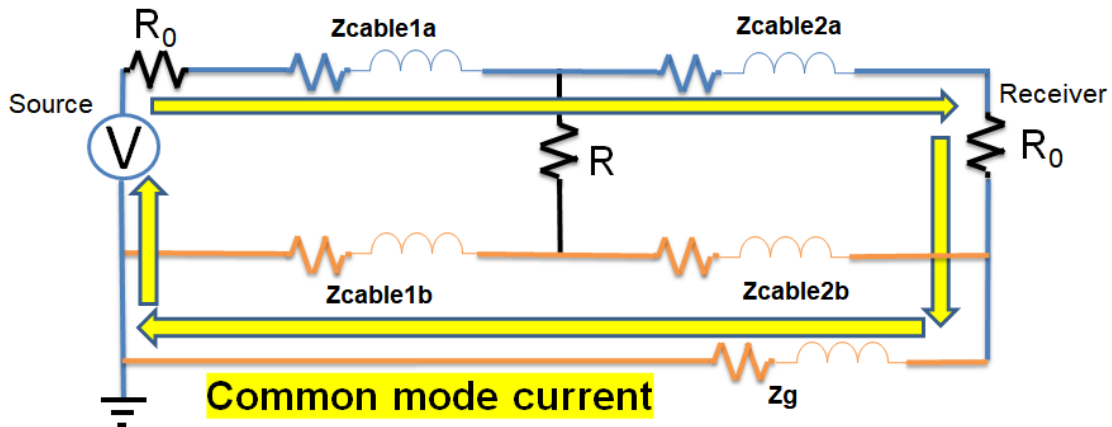


Figure 4: Common mode current path due to the ground loop.

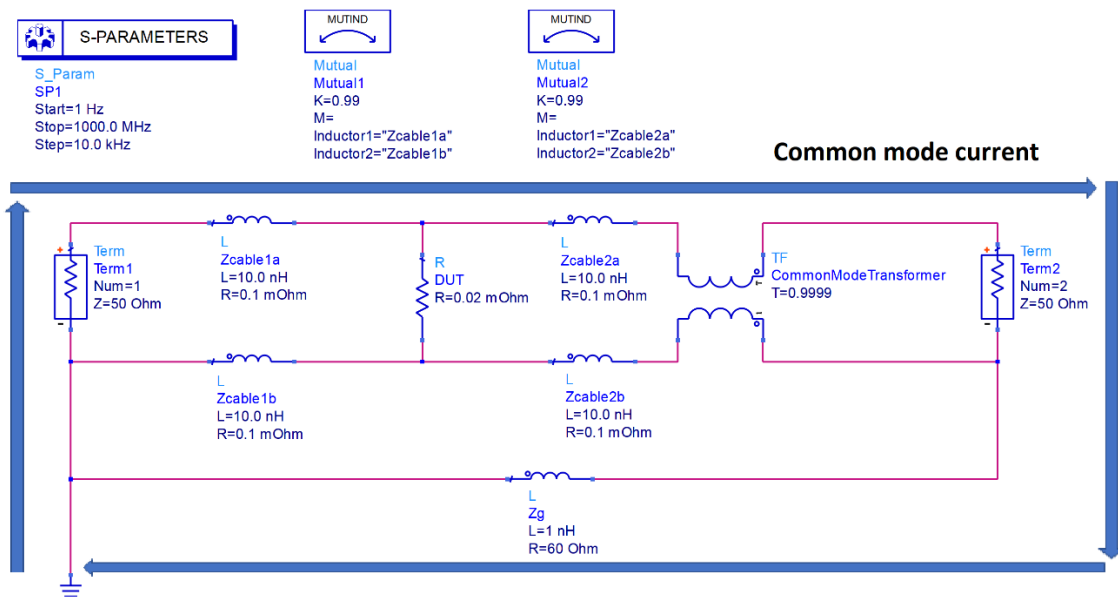


Figure 5: Keysight ADS example to estimate the ground loop error with and without common mode transformer depicting the common mode current path.

Solutions to ground loop problem

The common mode current should be minimized to minimize the measurement error. Picotest offers two solutions to minimize common mode current:

1. Common mode transformer - [J2102A](#)
2. Semi-floating differential amplifier - [J2113A](#)

The [J2113A](#) can be used at and above DC frequencies, and at voltages from -1.9V to +1.9V, while the [J2102A](#) is effective at and above 100 Hz. At frequencies above a few kHz, the common mode rejection ratio (CMRR) of the [J2102A](#) is significantly higher than that of the [J2113A](#). In most cases, the [J2102A](#) is a better choice for measuring ultra-low impedance ($20\ \mu\Omega$). The [J2113A](#) can be used to measure impedance at and above $1\ \text{m}\Omega$ and at frequencies down to DC. [Figure 5](#) shows Keysight ADS simulations for four cases,

1. Ground impedance, $Z_g = 1\ \text{nH} + 0.1\ \text{m}\Omega$, Common mode transformer, $T = 0$
2. Ground impedance, $Z_g = 1\ \text{nH} + 60\ \Omega$, Common mode transformer, $T = 0$
3. Ground impedance, $Z_g = 1\ \text{nH} + 0.1\ \text{m}\Omega$, Common mode transformer, $T = 0.9999$
4. Ground impedance, $Z_g = 1\ \text{nH} + 60\ \Omega$, Common mode transformer, $T = 0.9999$

The simulation results are shown in [Figure 6](#). [E5061B](#) has an inbuilt ground isolation amplifier that mimics of $60\ \Omega$ ($30\ \Omega$ per port) [[3](#), Figure 21] to improve the CMRR of the VNA. [Figure 6](#) shows that this is not good enough when we measure ultra low impedance ($20\ \mu\Omega$). Cases 3 and 4 shows that when a high-quality common mode transformer is present, good results can be achieved for measurements as low as $20\ \mu\Omega$.

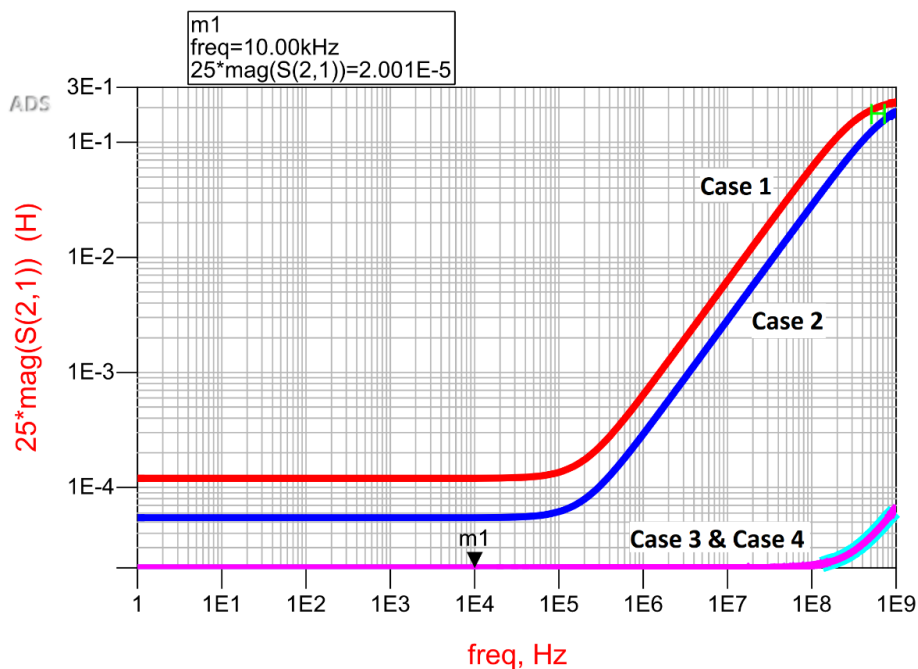


Figure 6: Keysight ADS simulation for four cases of [Figure 5](#) - 1) Ground impedance, $Z_g = 1\ \text{nH} + 0.1\ \text{m}\Omega$, Common mode transformer, $T = 0$; 2) $Z_g = 1\ \text{nH} + 50\ \Omega$, $T = 0$; 3) $Z_g = 1\ \text{nH} + 0.1\ \text{m}\Omega$, $T = 1$; 2) $Z_g = 1\ \text{nH} + 50\ \Omega$, $T = 1$ showing the need for common mode transformer even with $60\ \Omega$ (Z_g of $30\ \Omega$ per port) provided internally by the isolation amplifier [E5061B](#) [[3](#), Figure 21] while measuring ultra low impedances ($20\ \mu\Omega$).

Making Connections

High fidelity measurement requires high quality cables and probes, with high shielding effectiveness. Sometimes it is also important to AC couple the measurement in order to minimize DC loading or due to the operating voltage of the measurement exceeding the limits of the VNA. The Picotest [PCK01](#) is a high-performance cable and connector kit while the Picotest [P21B01](#) includes high-quality probes and DC Blocks. The highest accuracy when measuring bulk and decoupling capacitors is achieved by mounting the component on a characterized printed circuit board. The Picotest [DTBK01](#) kit includes most standard sizes and includes de-embedding data to remove parasitics of the PCB from the measurement.

[Table 1](#) shows a comparison of various cable characteristics. Picotest cables provide the best compromise for ultra-low impedance measurements in terms of loss, flexibility, and shielding characteristics. Picotest cables are made especially for accurate, 2-port impedance measurement.

Cable	R m/ft	Dia (in)	Fmax (GHz)	L (nH/ft)	C (pf/ft)	Shield	Comments
LMR400	1.65	0.405	5.8	60.0	24	100%	Excellent, but very bulky
RG316DS	3.95	0.186	3.0	73.5	29.4	99%	Very Good, bulky and stiff
RG405/AL	4.20	0.086	18	73.8	29.5	100%	Formable, but stiff
LMR240	4.50	0.24	5.8	60.0	24	84%	Bulky, flexible, poor shield
PICOTEST	4.70	0.102	5	71.8	28.7	100%	Ultra-flexible, triple shield
RG58	5.00	0.195	5	72.0	28.8	78%	Bulky, very poor shield
RG174	7.49	0.1	1	77.0	30.8	90%	Flexible
RG405	8.20	0.086	>33	73.8	29.5	100%	Double shield, semi-rigid
RG316	8.84	0.113	3	73.5	29.4	95%	Flexible
LMR100	9.50	0.1	8	77.0	30.8	90%	Flexible, poor shield

Table 1: Comparisons of various cables for ultra-low impedance measurements. PICOTEST cables are the best option for low impedance measurements based on flexibility, losses and shielding characteristics.

Measurement Examples

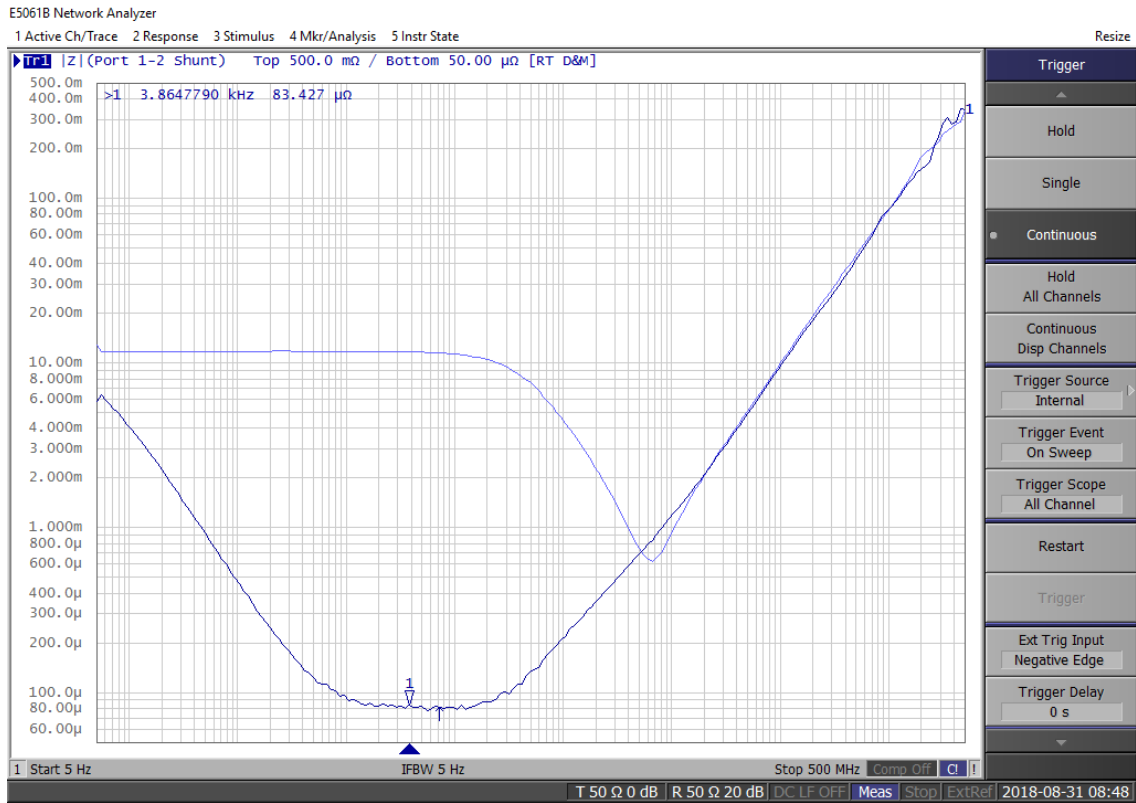


Figure 7: Comparisons of Picotest solutions for ground loop problem in 2-port shunt-through impedance measurements while measuring an $88 \mu\Omega$ resistance with and without ground loop isolator. NOTE: The fixture removal calibration is not performed in order to show the isolator performance. [J2102A](#) is not effective below 100 Hz. In this example the start frequency is 5 Hz showing this practical difficulty, whereas [Figure 6](#) is an ideal common mode transformer simulation not showing this practical limitation.

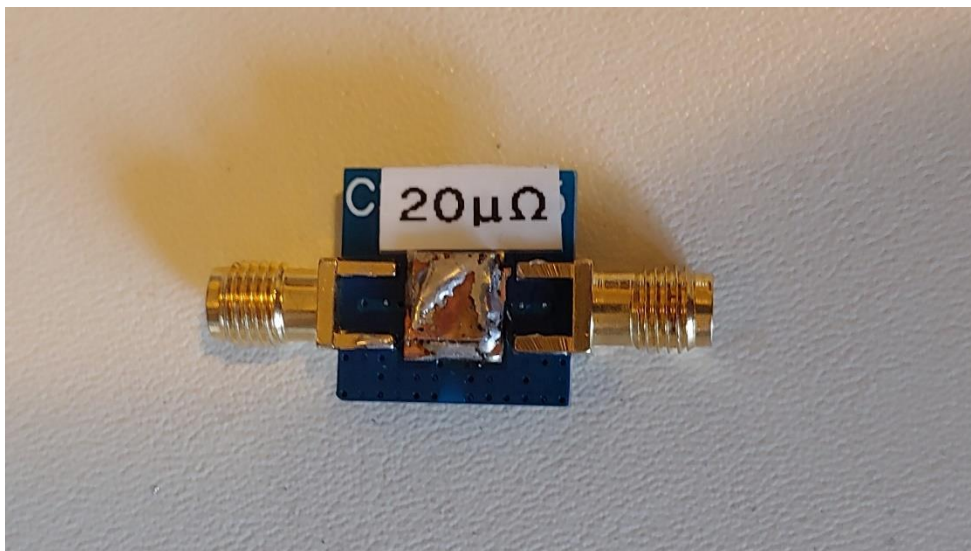


Figure 8: 20 $\mu\Omega$ resistance mounted on a fixture prior to measurement.

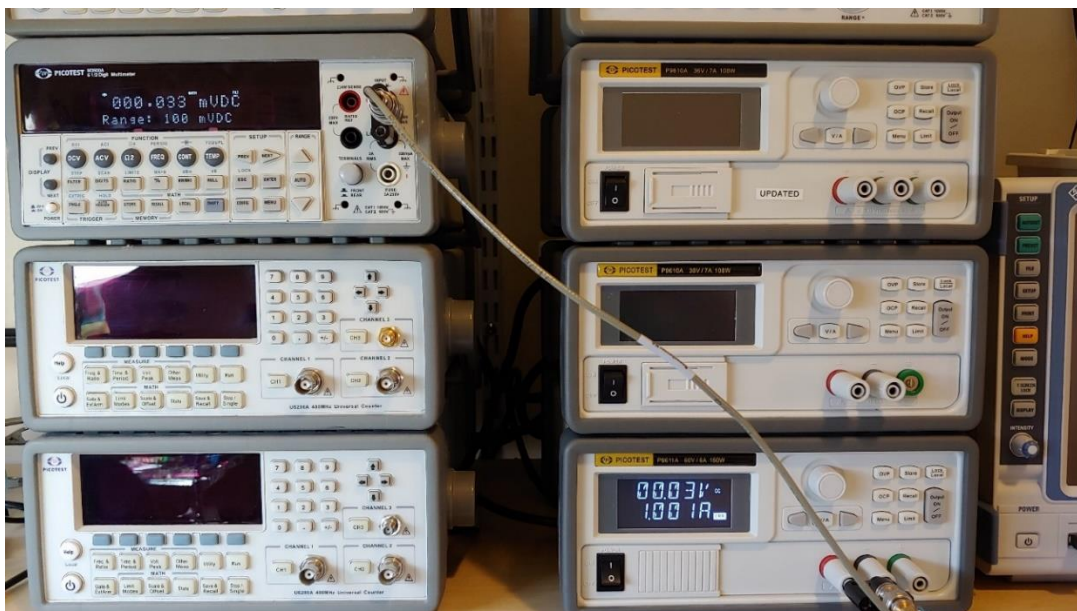


Figure 9: Set up to verify the DC resistance value using 4 wire kelvin method. Here 33 $\mu\Omega$ sample is tested.

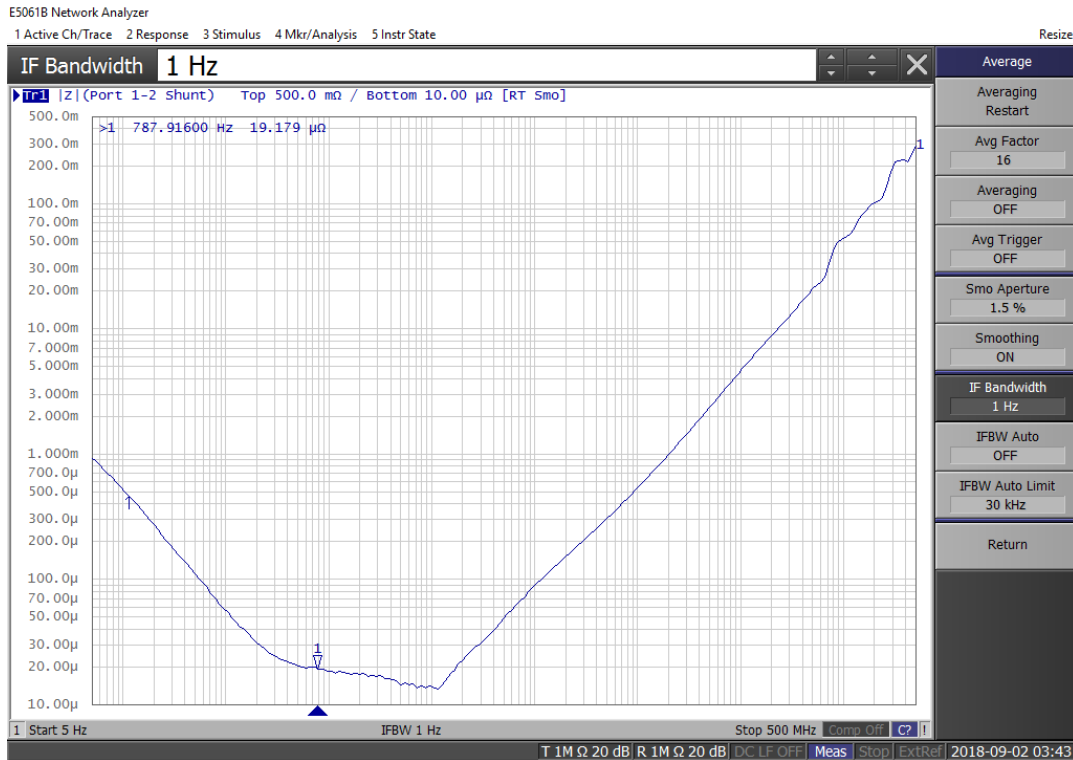


Figure 10: Measured $20 \mu\Omega$ resistance. NOTE: The fixture removal calibration is not performed in order to show the isolator performance. [J2102A](#) is not effective below 100 Hz. In this example the start frequency is 5 Hz showing this practical difficulty.

[Figure 7](#) shows the comparison of the measured impedance with and without the Picotest ground loop isolator [J2102A](#) while measuring an $88 \mu\Omega$ resistance. [Figure 8](#) shows the $20 \mu\Omega$ sample mounted on a fixture for measurements. All the measurements in this article use similar custom made samples mounted on similar fixtures. [Figure 9](#) shows the sample verification at DC by employing 4 wire kelvin measurement for the $33 \mu\Omega$ sample.

[Figure 10](#) show the experimental results of the measured $20 \mu\Omega$ sample. Cable losses and CMRR of the ground loop breaker are important sources of error in this ultra-low impedance measurement [5]. High quality cables and Picotest [J2102A](#) having very high CMRR are used in these measurements to overcome the errors.

Conclusion

This application note studied the fundamental reason behind the existence of inherent ground loop in a 2-port shunt-through impedance measurement system. Common mode current flowing through the measurement system introduces an error in the received signal in the VNA, and is erroneously sensed as an increase in the resistance of the DUT. The Picotest [J2102A](#) or [J2113A](#) products eliminate the ground loop in any commercial VNA used to measure impedance in the 2-port shunt-through configuration. [J2113A](#) is effective in isolating grounds when we are measuring impedances at and above 1 m Ω . [J2113A](#) can be used to isolate grounds at and above DC whereas [J2102A](#) can be used to isolate grounds at and above 100 Hz. [J2102A](#) can be used to measure impedances at and above $20 \mu\Omega$. In this article, measurement result is presented for $20 \mu\Omega$.

Measuring ultra-low impedance requires high quality cables, and the Picotest cables are made specifically for these applications. It is important to start with a known value of resistance in any measurements to validate the setup. In this application note, a 4 wire kelvin measurement is used to verify the measurement sample at DC.

Similar ground loops are present in other instruments and test setups, and the Picotest ground isolators are effective there as well. For additional information and products please visit <https://www.picotest.com/measurements/2-portUltralowImpedance.html>

References

- [1] R. W. Anderson, “S-parameter techniques for Faster, More Accurate Network Design,” *HP Appl. note 95-1*, Feb. 1967.
- [2] S. M. Sandler, “Extending the usable range of the 2-port shunt through impedance measurement,” *IEEE MTT-S Lat. Am. Microw. Conf. (LAMC)*, pp. 1–3, Dec 2016.
- [3] “Measuring Frequency Response with the Keysight E5061B LF-RF Network Analyzer,” *Keysight Technol. Appl. note*.
- [4] P. Carrier, “Signal integrity and power integrity in highspeed design,” *EDN*, 2014.
- [5] S. M. Sandler, “How to measure ultra-low impedance (100uOhm and lower) PDNs,” *EDICON*, Oct. 2018.