

# Evaluation of Gallium Nitride HEMTs for VRM Designs

Venkatesh Avula, University of Idaho  
Steve Sandler, Picotest

# Evaluation of Gallium Nitride HEMTs for VRM Designs

Venkatesh Avula, University of Idaho  
Steve Sandler, Picotest

# SPEAKERS

## Venkatesh Avula

*Graduate Student, University of Idaho*

avul3832@vandals.uidaho.edu | [www.linkedin.com/in/signalpowerintegrity](http://www.linkedin.com/in/signalpowerintegrity)

Venkatesh Avula is pursuing graduate study and research at the University of Idaho. He has 10 years of experience in signal integrity, power delivery analysis, and characterization of PCB, package and on-chip interconnects at various companies, including Seagate (formerly Avago/LSI) and Tektronix.



## Steve Sandler




*Managing Director, Picotest*

steve@picotest.com | [www.picotest.com](http://www.picotest.com)

Steve Sandler has more than 35 years' experience in the design, analysis, and troubleshooting of power conversion and system level equipment for commercial, military, and space applications. Steve is the CEO of Picotest.com, a company that designs and distributes test equipment accessories designed for test and troubleshooting power systems. Steve is also the founder and chief engineer of AEI Systems, a leading analysis and modeling company specializing in worst case analysis of high reliability systems. Steve has authored several books related to power electronics including most recently the book entitled "Power Integrity - Measuring, Optimizing and Troubleshooting Power Systems."


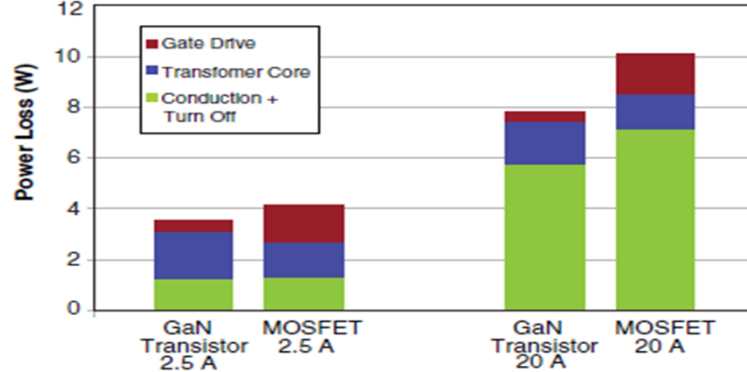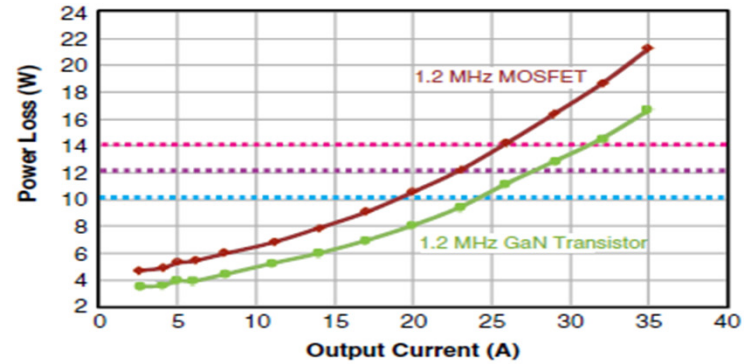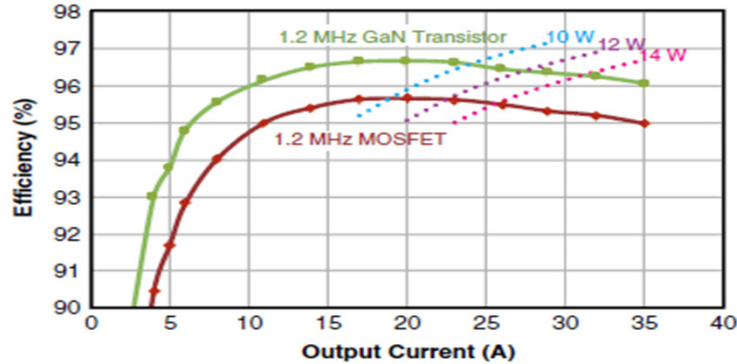
# Evaluation of Gallium Nitride HEMTs for VRM Designs




Example-48V to 12V bus converters operating at a switching frequency of 1.2MHz


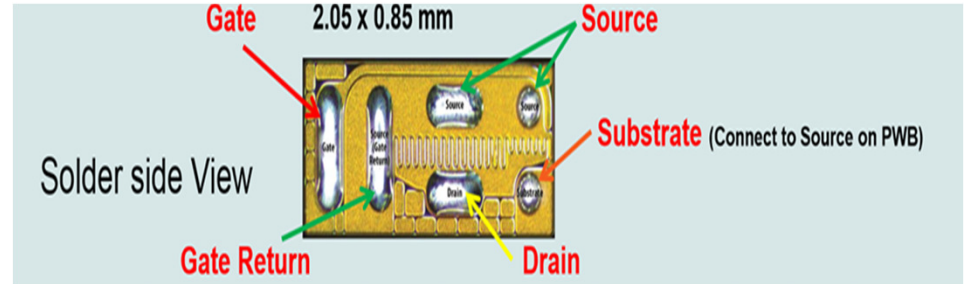
# Outline

- **Challenges in VRM design:**
  - Power delivery performance
  - Cost and space
- **Can eGaN solve these challenges?**
  - Material properties
  - Electrical properties
- **Incremental adoption of GaN**
  - Migrating a linear regulator design
  - Migrating a switching regulator design
- **Conclusion**




Part Number	Package (mm)	$V_{DS}$ (V)	$V_{GS}$ (V)	$R_{DS(on)}$ @5 V (m $\Omega$ )	$Q_G$ @5 V Typ. (pC)	$Q_{GS}$ Typ. (pC)	$Q_{GD}$ Typ. (pC)	$R_G$ (Ω)	$V_{th}$ (V)	$Q_{RR}$ (nC)	$I_D$ (A)	$T_J$ Max. (°C)
<a href="#">EPC8004</a>	LGA 2.05x0.85	40	6	125	358	110	31	0.34	1.4	0	2.7	150
<a href="#">EPC8009</a>	LGA 2.05x0.85	65	6	138	380	116	36	0.3	1.4	0	2.7	150
<a href="#">EPC8010</a>	LGA 2.05x0.85	100	6	160	354	109	32	0.3	1.4	0	2.7	150


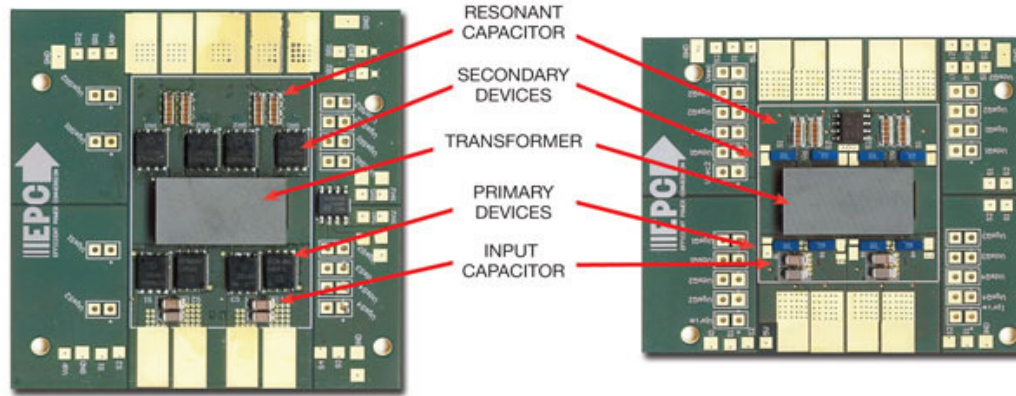
# Challenges in VRM design

- **Need of the hour: squeeze more and more features into less board space**
  - eGaN offers to solve this conundrum of cost and space.
  - Example-48V to 12V bus converters operating at a switching frequency of 1.2MHz





(a) Si MOSFET

(b) GaN HEMT

- **For existing Si FET based VRM designs, can we improve by supplanting with eGaN?**

# Evolution of Transistor devices

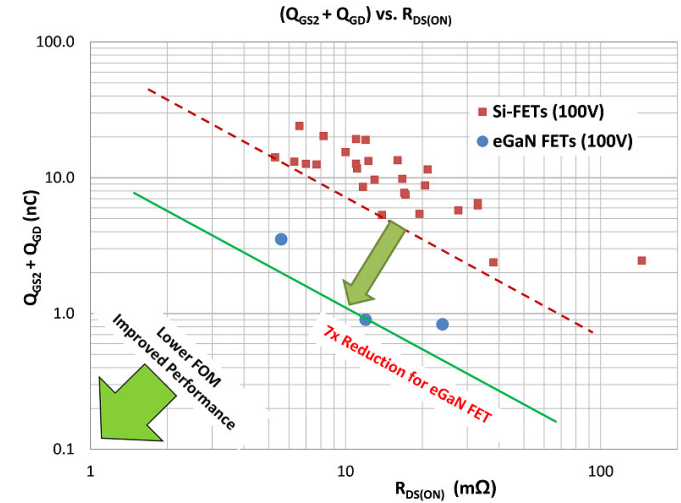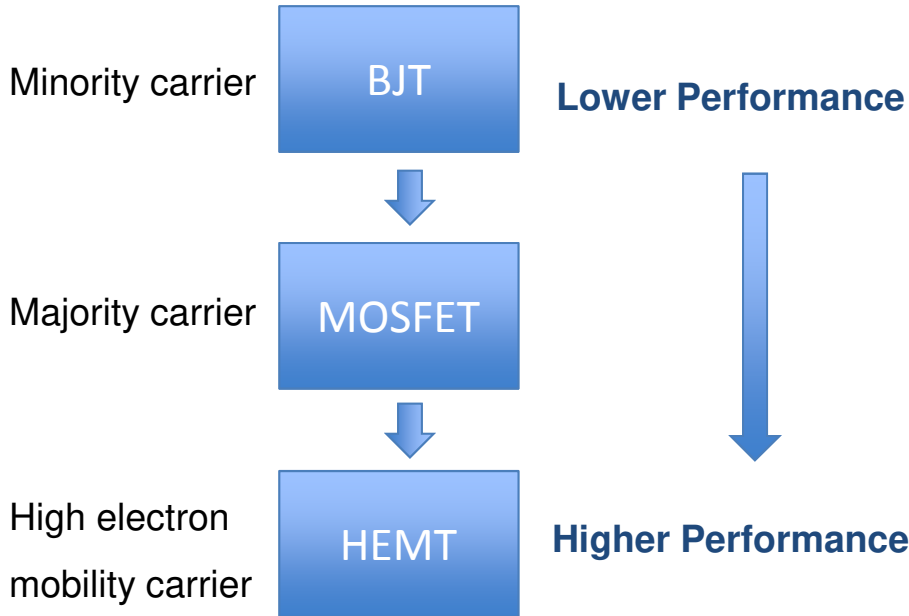

Switching - Figure of merit



# GaN vis-a-vis Silicon FET: material properties

- **Higher band gap:**
  - Results in lower leakage current.
  - Allows higher temperature operating capability.
- **Higher Critical field:**
  - Results in higher drain-source breakdown voltage.
- **Higher mobility:**
  - Results in lower Rds-on resistance, thereby lower conduction losses during power conversion.

Parameter	Silicon	GaN
Band Gap $E_g$ (eV)	1.12	3.39
Critical Field $E_{crit}$ (MV/cm)	0.23	3.3
Electron Mobility $\mu_n$ (cm <sup>2</sup> /V.s)	1400	1500
Permittivity $\epsilon_r$ (F/m)	11.8	9





# GaN vis-a-vis Silicon FET: electrical properties

- **Lower Rds-on:**
  - Lower conduction loss, higher conversion efficiency.
- **Lower leakage current:**
  - Lower leakage losses.
- **Lower capacitance:**
  - Allows faster switching speed.
  - Also lower gate charge required to turn on.
- **Lower Gate drive voltage margin:**
  - 1V margin for eGaN – a tight requirement.
- **Packaging:**
  - Much smaller.
- **Radiation tolerance:**
  - Inherently more radiation tolerant.

Parameter	Silicon MOSFET (Infineon BSC060N10NS3G)	eGaN HEMT (EPC2001)
Leakage current	1000 $\mu$ A	300 $\mu$ A
On-resistance	6.6 m $\Omega$	5.6 m $\Omega$
Capacitance	3700 pF	850 pF
Gate Charge $Q_G$	51 nC	8 nC
Diode forward voltage, $V_{SD}$	0.8V	1.75V
Reverse recovery charge $Q_{rr}$	6.4 $\mu$ C	54 nC
Reverse recovery time $t_{rr}$	630 ns	30 ns
Transconductance $G_{fs}$	85 S	100 S
Source-Drain Forward Voltage, $V_{SD}$	1 V	1.75 V
Threshold voltage change over temperature 25 <sup>o</sup> to 125 <sup>o</sup>	38% decrease	3% increase
Maximum Switching speed	<1MHz	100s of MHz
Package size	6.3 x 5.0 mm	4.1 x 1.6 mm



# Linear regulators: figures of merit


- **Linear regulators:**
  - primarily used in applications, at lower operating current levels.
  - or those applications where voltage rail noise must be kept to a minimum.
- **Significant figures of merit:**
  - output impedance
  - dropout voltage (headroom)
  - PSRR

Regulator FOM	Key Pass Device Parameters	Si MOSFET	eGaN HEMT	Winner
Output Impedance	Transconductance	Lower	Higher	eGaN
Dropout Voltage	$R_{DSon}$	Higher	Lower	eGaN
PSRR	Junction Capacitance	Higher	Lower	eGaN
Noise	Junction Noise	Higher	Lower	eGaN
Physical Size	Electron Mobility Breakdown Field	Lower Lower	Higher Higher	eGaN eGaN
Radiation Tolerance	Radiation Hardening	Not Hard	Hard	eGaN
Junction Temperature	$R_{theta}$	Lower	Higher	Si



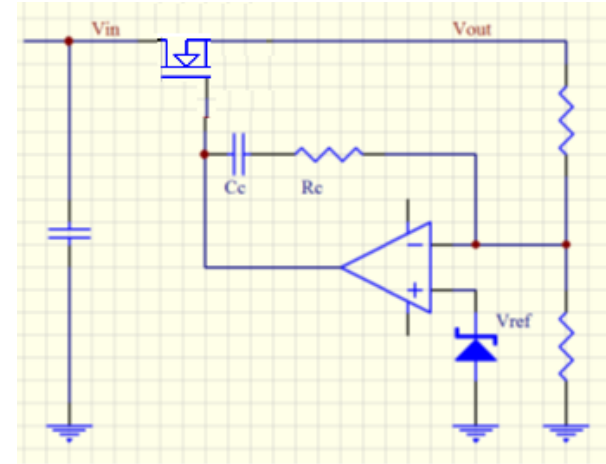
# Linear regulators: migration path

- **The migration path is simple with few concerns:**
  - The gate source voltage must be kept below 5V or the eGaN HEMT device can be damaged.
  - Only N-channel designs can be migrated as there are no P-channel eGaN HEMT devices.
  - Sufficient cooling to account for the higher thermal resistance resulting from the smaller size of the eGaN HEMT device.




# Linear regulators: migration path example

Si FET based

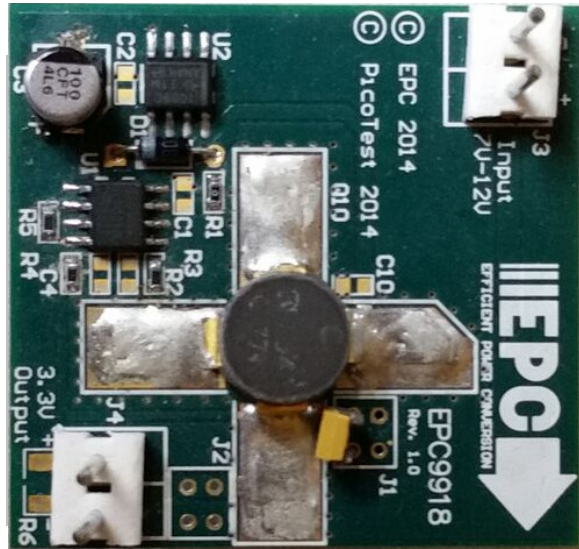

vs.

eGaN based

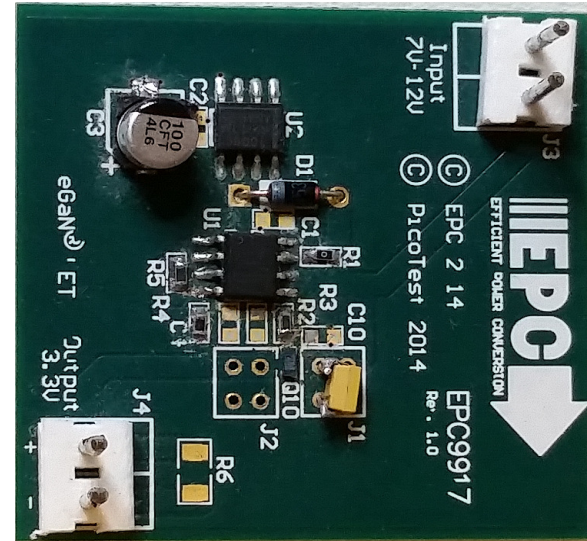

- **Smaller design: Space saver**



# Linear regulators: output impedance

- Regulator impedance depends on pass transistor's transconductance and loop gain:


- Transistor device's dynamic junction resistance,  $R_j = \frac{NKT_k}{q I_{out}} = \frac{26mV}{I_{out}} N = 1/G f s$

- Loop gain, as a dominant pole and open loop DC gain,  $T = \frac{a Avol}{s+a}$

- Regulator impedance,  $Z_{reg} = R_j \frac{1}{(1+T)} = \frac{1}{Gfs} \frac{1}{(1+T)} = \frac{1}{Gfs} \frac{1}{\left(1 + \frac{a Avol}{s+a}\right)} = \frac{(s+a)}{Gfs \cdot a \cdot (Avol + 1) + s}$


- Output impedance, can be obtained by differentiating the regulator impedance,  $Z_{reg-AC} = \frac{\partial}{\partial s} \left[ \frac{(s+a)}{Gfs \cdot a \cdot (Avol + 1) + s} \right] = \frac{1}{Gfs \cdot a \cdot (G + 1) + s} - \frac{(s+a)}{Gfs \cdot (a \cdot (G + 1) + s)^2}$

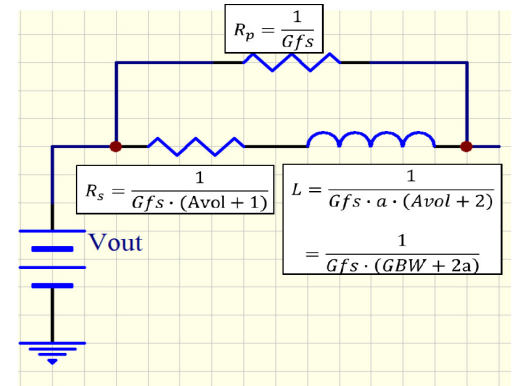- Since the transconductance of eGaN is much higher, linear regulator impedance is decreased by replacing Si with eGaN.



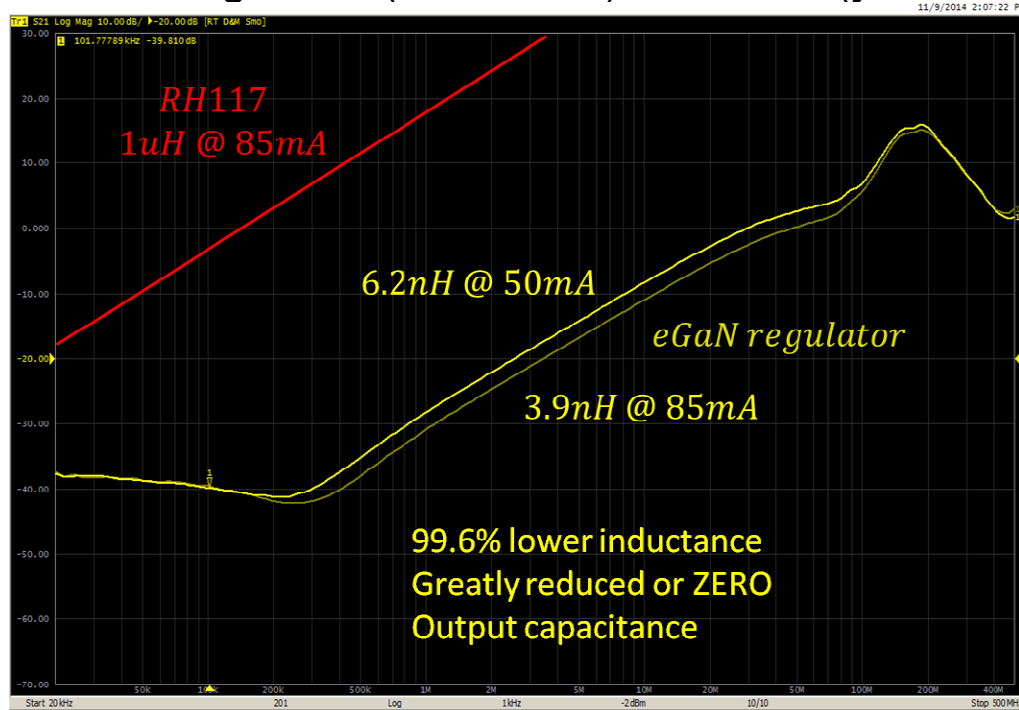
# Linear regulators: output impedance

Comparison of measured output impedance benefit from higher bandwidth Si three terminal regulator (Red trace) vs eGaN (yellow traces)



# Linear regulators: output impedance

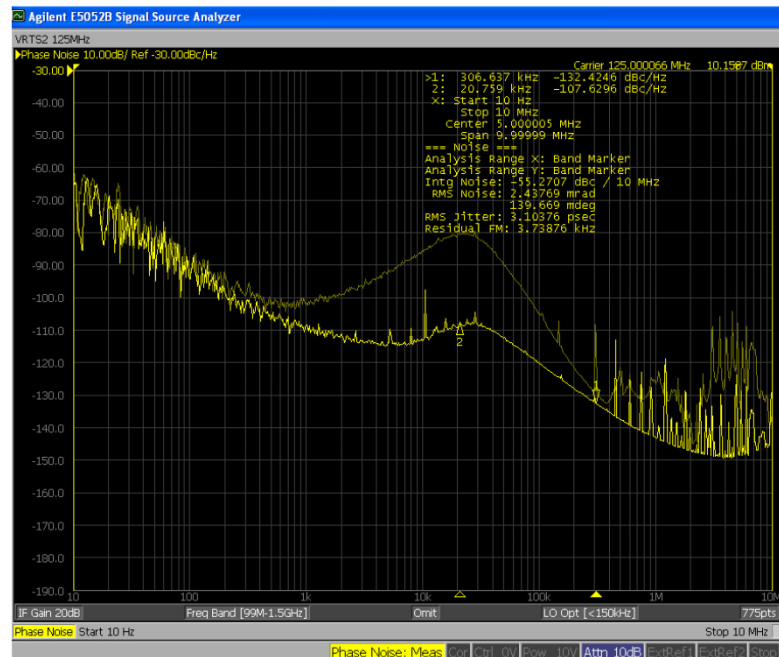

Comparison of measured phase noise of clock powered by linear regulators, Si LM317 (dim memory trace) vs eGaN (bright data trace)




# Linear regulators: Dropout voltage and PSRR

- **Dropout voltage**

- It is the minimum voltage drop across the regulator as it delivers the load current :  $V_{dropout} = I_{out} RDS_{on}$
- As eGaN offers lower  $RDS_{on}$ , the dropout voltage performance is improved with replacement of Si MOSFET device by eGaN.

- **Power supply ripple rejection ratio (PSRR)**

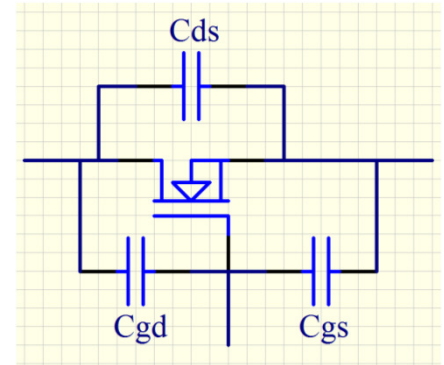- AC voltage fluctuations presented at the input to a regulator result in corresponding noise at the output,  $PSRR = \frac{\Delta V_{out}}{\Delta V_{in}}$
- PSRR is a measure of the ability to reject such input variations.
- Since eGaN HEMT offers significantly reduced junction capacitance compared to Si MOSFET, the PSRR performance is directly improved.



Transistor's equivalent capacitance model





# Switching regulators: figures of merit

- **Switching regulators:**

- Primarily for those at higher operating current levels or where efficiency is paramount.
- And where there is high voltage difference between input and output.

- **Significant figures of merit:**


- Efficiency
- Physical size
- Switch node waveforms
- EMI

Regulator FOM	Key Switch Device Parameters	Si MOSFET	eGaN HEMT	Winner
Efficiency	RDSon, Reverse conducting body diode drop, Package inductance, capacitance	Higher	Lower	eGaN
		Lower	Higher	Si
Gate drive voltage overshoot tolerance	Gate drive voltage margin	Higher	Lower	Si
		Lower	Higher	eGaN
Layout parasitic impact on performance	Gate drive voltage margins	Higher	Lower	Si
Temperature range	Temperature coefficient of RDSon and Vth	Higher	Lower	eGaN
Switch node waveform	Electron Mobility, Gate charge	Lower	Higher	eGaN
Switching frequency	Gate charge, Device capacitance	Higher	Lower	eGaN
		Higher	Lower	eGaN
Size	Package, need for external components	Bigger	Smaller	eGaN



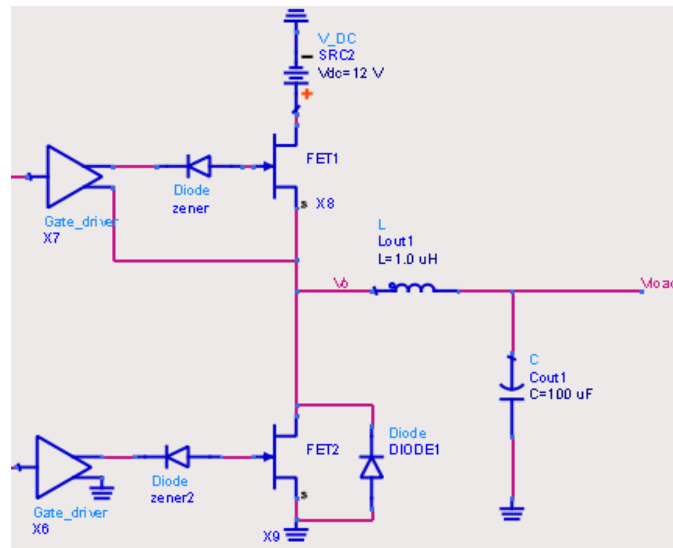
# Switching regulators: migration path

- **Migration is not trivial - several concerns**
  - If dead time is excessive,
    - Add Schottky diode.
    - Configure the gate controller to have least possible dead time.
    - Lesser the dead time, lesser the reversion conduction flow and higher the power conversion efficiency
  - If gate controllers have high gate drive voltage, as most do,
    - The gate-source voltage must be kept below 5V, or the eGaN HEMT device will be damaged.
    - Add reverse biased Zener diode to shift gate level to 5V



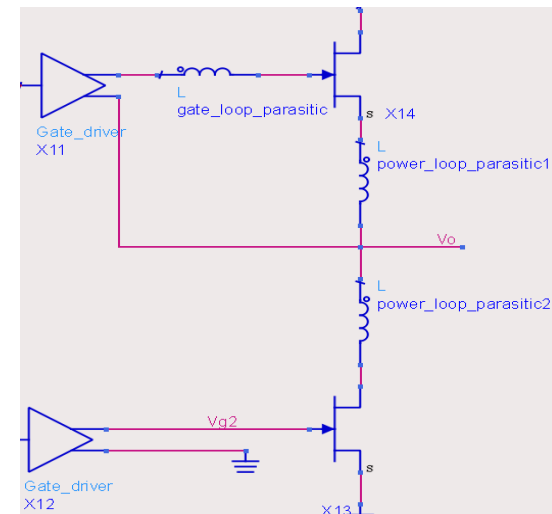
# Switching regulators: migration path

- **eGaN HEMT is susceptible to board layout parasitics**
  - eGaN HEMT is vulnerable to  $L di/dt$  and  $C dv/dt$  spikes, as it runs at higher  $di/dt$  and  $dv/dt$  rates.
  - Such overshoots at the gate drive can exceed the recommended 6V of eGaN HEMT, potentially damaging the device.
  - Also, overshoot voltages incur power loss.
  - Therefore, the PCB board layout needs to be optimized for suitable eGaN performance.




# Switching regulators: migration path

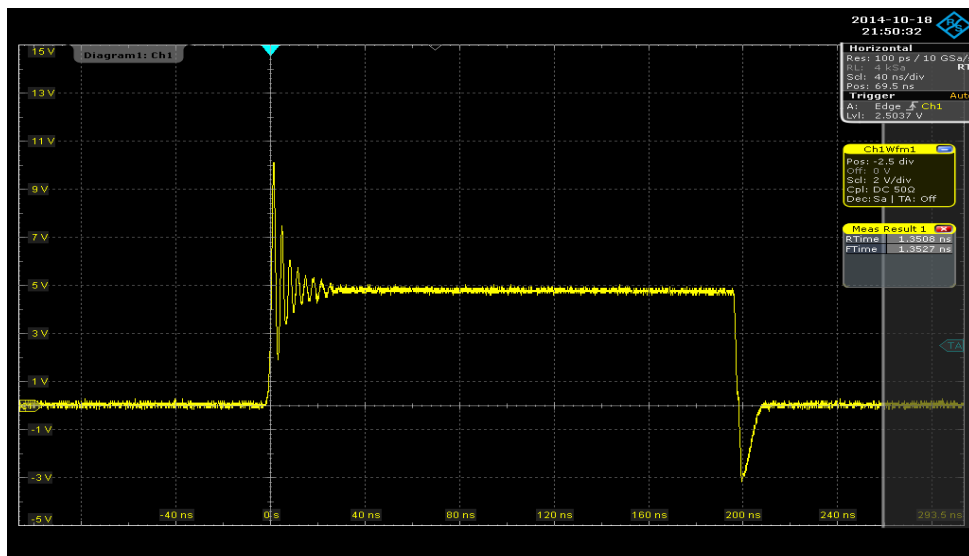

Higher speed eGaN devices can create significant ringing on the drain voltage generating EMI and increasing voltage stress


# Linear regulators: migration path example

Si FET based

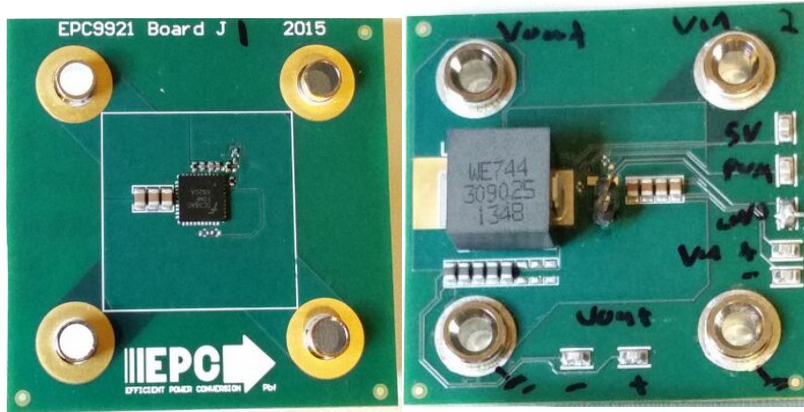

VS.

eGaN based

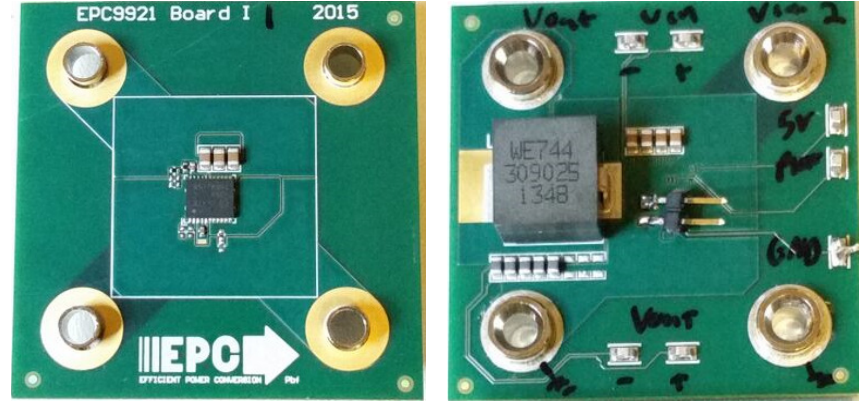

- **Smaller design: Space saver**



# Switching regulators: Efficiency



- **Power conversion efficiency depends on the dynamic power losses that occur during the transition of transistors from on to off and vice-versa.**
  - The total loss is lower in eGaN based switching regulator, provided the conduction loss is controlled.

Regulator Losses	Key Switch Device Parameters	Si MOSFET	eGaN HEMT	Winner
Switching loss	Gate charge	Higher	Lower	eGaN
Reverse conduction loss	Body diode drop	Lower	Higher	Si
Capacitance loss	Device capacitance	Higher	Lower	eGaN
Reverse recovery loss	Reverse recovery charge	Higher	Lower, nearly zero.	eGaN
Gate charge loss	Gate charge	Higher	Lower	eGaN


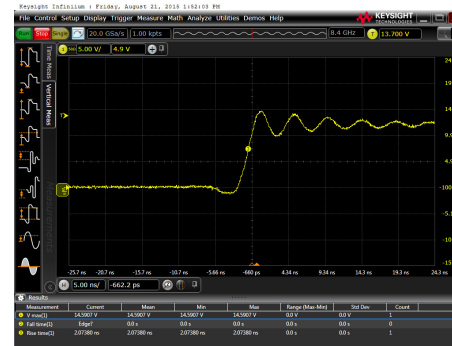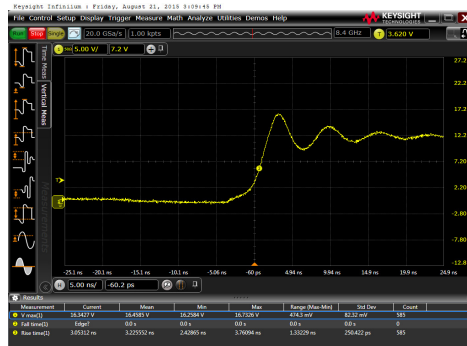
# Switching regulators: switching node waveforms

The eGaN waveform are found to have sharper transitions.




Fairchild DrMOS LTC3891

eGaN LTC3891
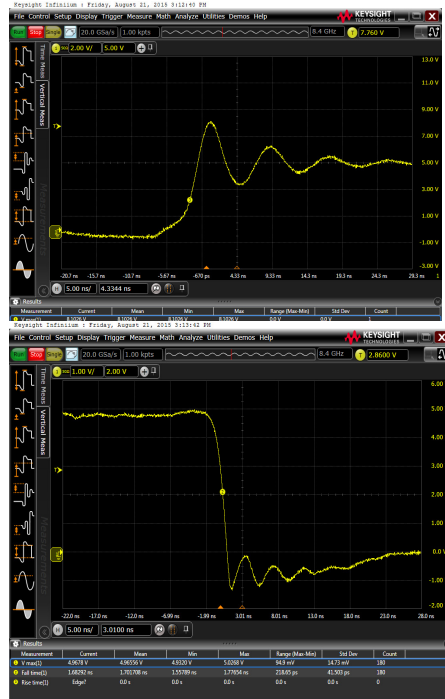
# Switching regulators: Gate drive voltage stability

The PCB layout parasitic inductance is minimized in order to keep the gate voltage below 6V.



Fairchild DrMOS LTC3891



eGaN LTC3891






# Switching regulators: EMI

Emissions are quite different for the eGaN HEMT and Si MOSFET devices, especially at the higher frequency.


Fairchild DrMOS LTC3891

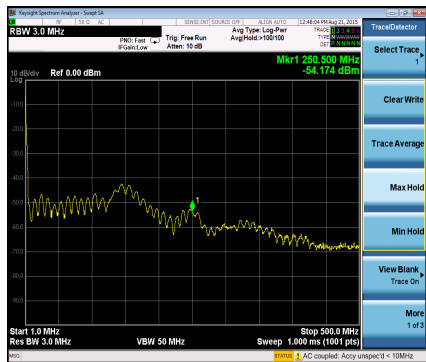

E field at Si MOSFET




H field at Si MOSFET

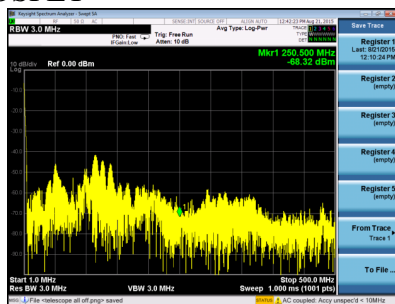


Telescopic Antenna

vs.


eGaN LTC3891

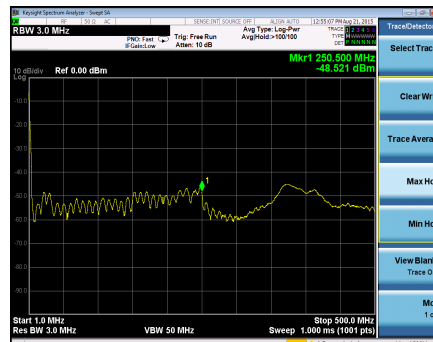

E field at eGaN HEMT

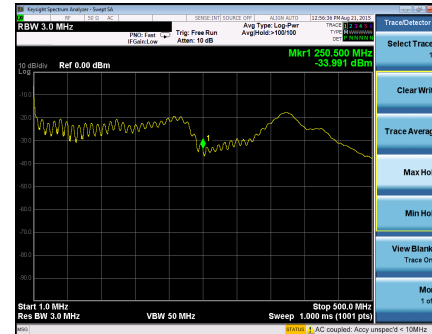

H field at eGaN HEMT

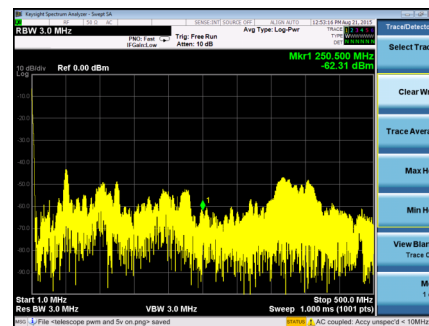

Telescopic Antenna



# Conclusion

- **Existing linear regulator designs can directly benefit from replacing the Si BJT or MOSFET with eGaN HEMT :**
  - As part of this migration, it is also possible to increase the operating bandwidth of the regulator further improving the performance.
  
- **For switching regulators, migration from Si MOSFET to eGaN HEMT is complex and we cannot take full advantage of eGaN technology simply by changing the switches from Si to eGaN.**
  - It is generally necessary to design it for eGaN from the start.
  - Optimized eGaN HEMT based switching regulator design will outperform a Si MOSFET based solution in most cases.



# Thank you!

---

## QUESTIONS?

